


**CHAPTER VIII**

**FINITE STATE MACHINES (FSM)**

- From the previous chapter we can make simple memory elements.
  - Latches as well as latches with control signals
  - Flip-flops
  - Registers
- The goal now is to use the memory elements to hold the running state of the machine.
  - The state of the machine can be used to perform sequential operations.
  - This chapter will discuss how to represent the state of the machine for design and communication purposes.


- **Mealy machine**

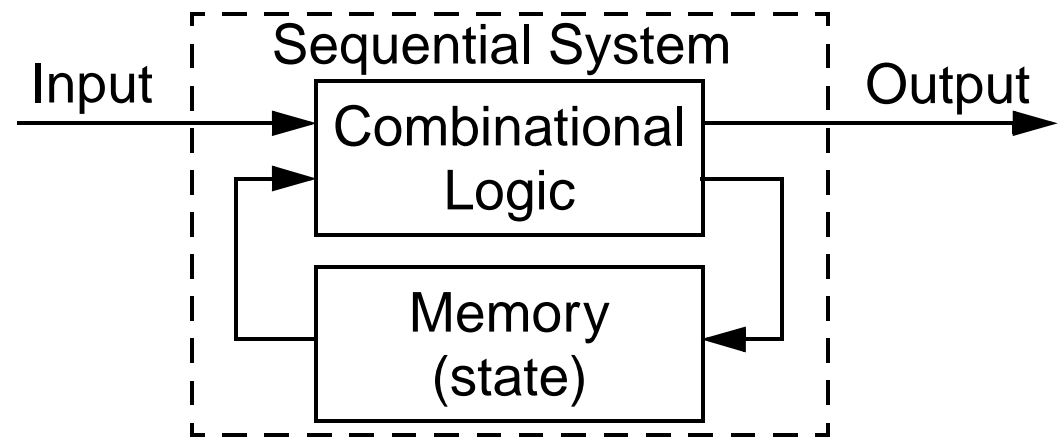- Sequential system where output depends on current input and state.




- **Moore machine**

 - Sequential system where output depends only on current state.



- **Synchronous sequential system**
  - Behaviour depends on the inputs and outputs at discrete instants of time.
  - Flip-flops, registers, and latches that are enabled/controlled with a signal derived from clock form a synchronous sequential system.
- **Asynchronous sequential system**
  - Behaviour depends on inputs at any instant of time.
  - Latches without control signals behave in an asynchronous manner.
- The state machines discussed in this chapter will be synchronous sequential systems (i.e. controlled by a clock)
  - This allows us to form timed Boolean functions such as
    - $\mathbf{N}(t) = \mathbf{D}_A(t + 1)$  where  $\mathbf{N}$  is the next state of a D flip-flop  $\mathbf{D}_A$ .

 - A state diagram represents a finite state machine (FSM) and contains
  - **Circles:** represent the machine states
    - Labelled with a binary encoded number or  $S_k$  reflecting state.
  - **Directed arcs:** represent the transitions between states
    - Labelled with input/output for that state transition.




Input:  $x(t) \in \{a, b\}$   
Output:  $z(t) \in \{p, q\}$   
State:  $s(t) \in \{S_k, S_j\}$   
Initial state:  $s(0) = S_k$

- Some restrictions that are placed on the state diagrams:
  - FSM can only be in **one state at a time!**
    - Therefore, only in one state, or one circle, at a time.
  - State transitions are followed only **on clock cycles.** (synchronous!)
- Mealy machines and Moore machines can be labelled differently.
  - **Mealy machine:** Since output depends on state and inputs:
    - Label directed arcs with **input/output** for that state transition.
  - **Moore machine:** Since output depends only on state:
    - Label directed arcs with **input** for that state transition.
    - Label state circles with  $S_k$ /**output**.

# STATE DIAGRAMS

 
## STATE DIAGRAM EXAMPLES

- The following is a simple example. What does this state machine do?



Input:  $x(t) \in \{0, 1\}$   
Output:  $z(t) \in \{0, 1\}$   
State:  $s(t) \in \{S_0, S_1\}$   
Initial state:  $s(0) = S_0$

 - Here is a simplified way of forming the above state machine.




- An input of 0 or 1 causes the transition with output 1 and 0, respectively.


# STATE DIAGRAMS
 
## BIT FLIPPER EXAMPLE

- Consider the simple bit flipper looked at the in previous chapter. How would a state diagram be formed?
- Below is one possible way of drawing the state diagram for the bit flipper.



 - Since the bit flipper is a Moore machine, the state diagram can also be





# STATE DIAGRAMS

## PATTERN DETECT EXAMPLE

- Suppose we want a sequential system that has the following behaviour

Input:  $x(t) \in \{0, 1\}$

Output:  $z(t) \in \{0, 1\}$

Function: 
$$z(t) = \begin{cases} 1 & \text{if } x(t-3, t) = \mathbf{1101} \\ 0 & \text{otherwise} \end{cases}$$


- Effectively, the system should output a **1** when the last set of four inputs have been **1101**.
- For instance, the following output  $z(t)$  is obtained for the input  $x(t)$

$t$	0123456789...
$x(t)$	1001001001001 <b>1101</b> 01 <b>1011</b> 0100 <b>1101</b> 001 <b>101</b> 001
$z(t)$	???0000000000000 <b>1</b> 0000 <b>1</b> 00100000 <b>1</b> 000

# STATE DIAGRAMS

 
## PATTERN DETECT EXAMPLE

- The following state diagram gives the behaviour of the desired 1101 pattern detector.
- Consider  $S_0$  to be the initial state,  $S_1$  when first symbol detected (1),  $S_2$  when subpattern **11** detected, and  $S_3$  when subpattern **110** detected.



- State tables also express a systems behaviour and consists of
  - Present state
    - The present state of the system, typically given in binary encoded form or with  $S_k$ . So, a state of  $S_5$  in our state diagram with 10 states would be represented as 0101 since we require 4 bits.
  - Inputs
    - Whatever external inputs used to cause the state transitions.
  - Next state
    - The next state, generally in binary encoded form.
  - Outputs
    - Whatever outputs, other then the state, for the system. Note that there would be no outputs in a Moore machine.

 - Consider again the bit flipper example with state diagram



- The state table for this state diagram would be

<u>Present State</u>	<u>Input</u>	<u>Next State</u>	<u>Output</u>
$S_0$ or <b>0</b>	-	<b>1</b>	-
$S_1$ or <b>1</b>	-	<b>0</b>	-

- From a state diagram, a state table is fairly easy to obtain.
  - Determine the number of states in the state diagram.
  - If there are  $m$  states and  $n$  1-bit inputs, then there will be  $m2^n$  rows in the state table.
    - Example: If there are 3 states and 2 1-bit inputs, each state will have  $2^2 = 4$  possible inputs, for a total of  $3*4=12$  rows.
  - Write out for each state, the  $2^n$  possible input rows.
  - For each state/input pair, follow the directed arc in the state diagram to determine the next state and the output.

# STATE TABLES


## PATTERN DETECT EXAMPLE

- If we consider the pattern detection example previously discussed, the following would be the state table.

Present State	Input		Next State	Output		
	$P_1$	$P_0$			$X$	
			$N_1$	$N_0$	$Z$	
$S_0$ or	0	0	0	$S_0$ or	0	0
$S_0$ or	0	0	1	$S_1$ or	0	1
$S_1$ or	0	1	0	$S_0$ or	0	0
$S_1$ or	0	1	1	$S_2$ or	1	0
$S_2$ or	1	0	0	$S_3$ or	1	1
$S_2$ or	1	0	1	$S_2$ or	1	0
$S_3$ or	1	1	0	$S_0$ or	0	0
$S_3$ or	1	1	1	$S_1$ or	0	1

- If given a state table, the state diagram can be developed as follows.
- Determine the number of states in the table and draw a state circle corresponding to each one.
  - Label the circle with the state name for a Mealy machine.
  - Label the circle with the state name/output for a Moore machine.
- For each row in the table, identify the present state circle and draw a directed arc to the next state circle.
  - Label the arc with the input/output pair for a Mealy machine.
  - Label the arc with the input for a Moore machine.

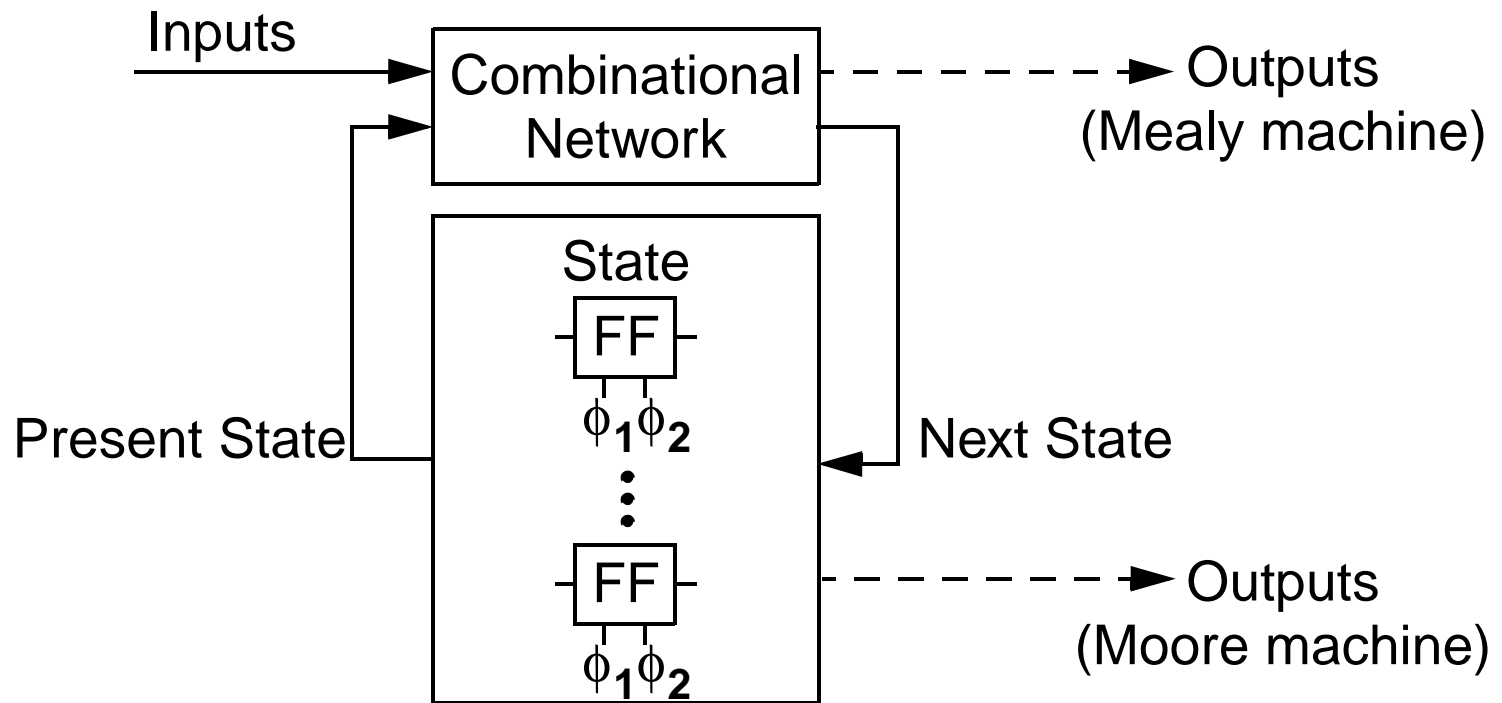- With the descriptions of a FSM as a state diagram and a state table, the next question is how to develop a sequential circuit, or logic diagram from the FSM.
- Effectively, we wish to form a circuit as follows.





- The procedure for developing a logic circuit from a state table is the same as with a regular truth table.
  - Generate Boolean functions for
    - each external outputs using external inputs and present state bits
    - each next state bit using external inputs and present state bits
  - Use Boolean algebra, Karnaugh maps, etc. as normal to simplify.
  - Draw a register for each state bit.
  - Draw logic diagram components connecting external outputs to external inputs and outputs of state bit registers (which have the present state).
  - Draw logic diagram components connecting inputs of state bits (for next state) to the external inputs and outputs of state bit registers (which have the present state).

# SEQ. CIRCUITS

## PATTERN DETECT EXAMPLE

- Following the procedure outlined, Boolean functions for the pattern detector state table can be formed using Karnaugh maps as follows.

		$P_1P_0$			
$X$		00	01	11	10
0	0	0	0	1	0
1	1	1	1	0	0

$N_1$

		$P_1P_0$			
$X$		00	01	11	10
0	0	0	1	0	0
1	1	1	0	1	0

$N_0$

		$P_1P_0$			
$X$		00	01	11	10
0	0	0	0	0	0
1	0	0	0	1	0

$Z$

$$N_1 = XP_1\bar{P}_0 + \bar{X}P_1P_0$$

$$N_0 = \bar{X}\bar{P}_1P_0 + XP_1P_0 + X\bar{P}_1\bar{P}_0 = \bar{X}\bar{P}_1P_0 + X(\bar{P}_1 \oplus P_0)$$

$$Z = XP_1P_0$$

- Notice that the previous Boolean functions can also be expressed with time as follows.

$$\mathbf{N}_1(t) = \mathbf{P}_1(t+1) = \mathbf{X}(t) \cdot \overline{\mathbf{P}_1(t)} + \overline{\mathbf{X}(t)} \cdot \mathbf{P}_1(t) \cdot \mathbf{P}_0(t)$$

$$\begin{aligned}\mathbf{N}_0(t) = \mathbf{P}_0(t+1) &= \overline{\mathbf{X}(t)} \cdot \overline{\mathbf{P}_1(t)} \cdot \mathbf{P}_0(t) + \mathbf{X}(t) \cdot \mathbf{P}_1(t) \cdot \mathbf{P}_0(t) \\ &\quad + \mathbf{X}(t) \cdot \overline{\mathbf{P}_1(t)} \cdot \overline{\mathbf{P}_0(t)} \\ &= \overline{\mathbf{X}(t)} \cdot \overline{\mathbf{P}_1(t)} \cdot \mathbf{P}_0(t) + \mathbf{X}(t) \cdot \overline{\mathbf{P}_1(t) \oplus \mathbf{P}_0(t)}\end{aligned}$$


$$\mathbf{Z}(t) = \mathbf{X} \cdot \mathbf{P}_1(t) \cdot \mathbf{P}_0(t)$$

- An important thing to note in these equations is the relation between the present states P and the next states N.

# SEQ. CIRCUITS
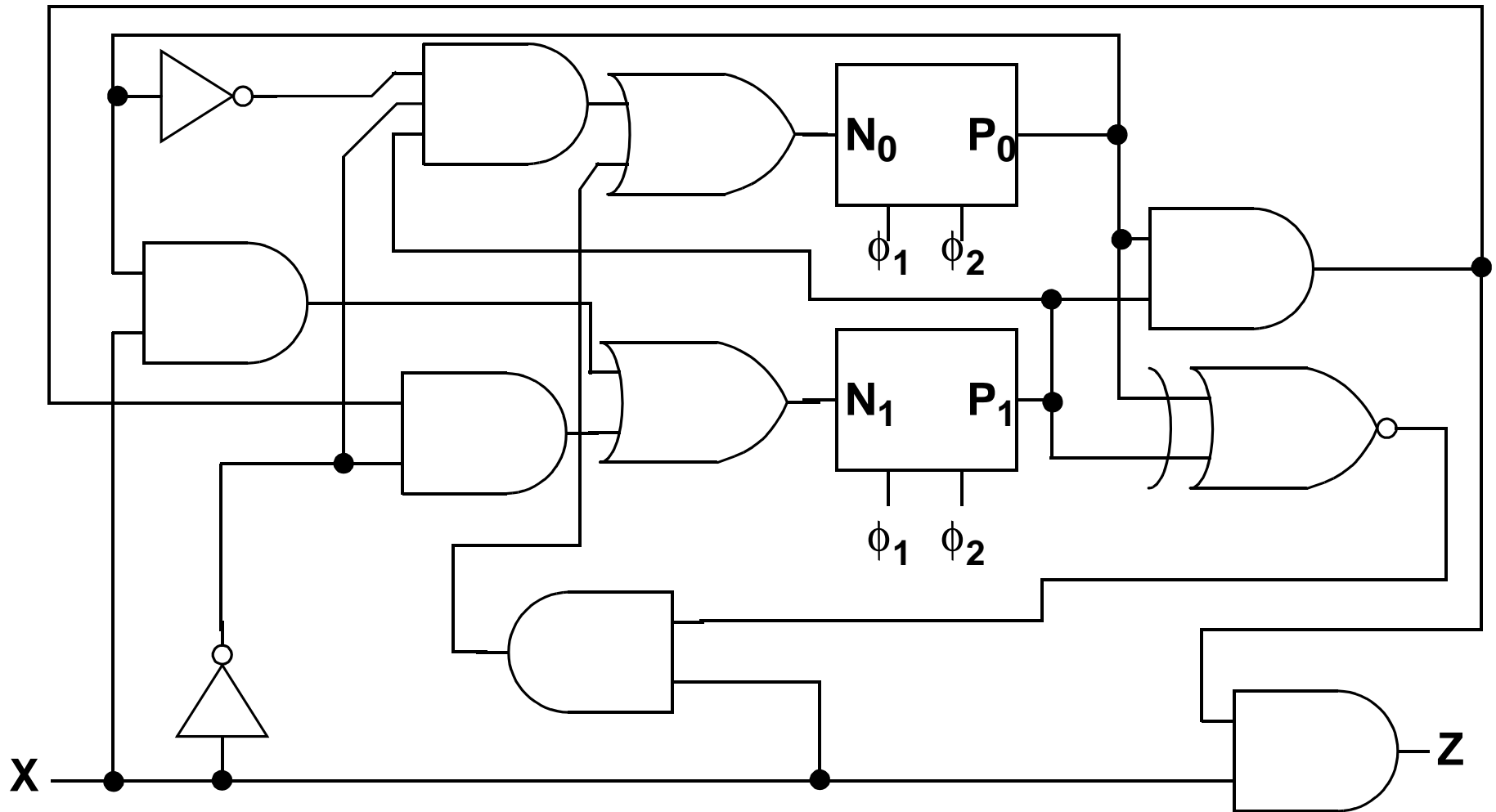
## PATTERN DETECT EXAMPLE

- The following logic circuit implements the pattern detect example.







- Consider the following system description.
  - A sequential system has
    - One input = {**a**, **b**, **c**}
    - One output = {**p**, **q**}
  - Output is
    - **q** when input sequence has even # of **a**'s and odd # of **b**'s
    - **p** otherwise

- We can begin forming a state machine for the system description by reviewing the possible states. In addition, assign each state a state name.
  - $S_{EE}$ : even # of **a**'s and even # of **b**'s / output is **p**
  - $S_{EO}$ : even # of **a**'s and odd # of **b**'s / output is **q**
  - $S_{OO}$ : odd # of **a**'s and odd # of **b**'s / output is **p**
  - $S_{OE}$ : odd # of **a**'s and even # of **b**'s / output is **p**
- Note that this machine can be a Moore machine. So, we can associate the output with each state.

# FSM EXAMPLES

## EXAMPLE #1


- Now draw a circle with each state.

    

# FSM EXAMPLES
 
## EXAMPLE #1

- Finally, for each state, consider the effect for each possible input.
- For instance, starting with state  $S_{EE}$ , the next state for the three input **a**, **b**, and **c** are determined as follows.






# FSM EXAMPLES
 
## EXAMPLE #1

- Finishing the state diagram, the following is obtained.



- A state table can also be formed for this state diagram as follows.
  - First, assign a binary number to each state
    - $S_{EE} = 00$ ,  $S_{EO} = 01$ ,  $S_{OO} = 10$ ,  $S_{OE} = 11$
  - Assign a binary number to each input
    - $\mathbf{a} = 00$ ,  $\mathbf{b} = 01$ ,  $\mathbf{c} = 10$
  - Assign a binary number to each output
    - $\mathbf{p} = 0$ ,  $\mathbf{q} = 1$
  - Then for each state, find the next state for each input. In this case there are three possible input values, so, three possible state transitions from each state.
- The state table on the following slide shows the results for this example.

# FSM EXAMPLES

## EXAMPLE #1

Present State		Input X	Next State		Output Z
P <sub>1</sub>	P <sub>0</sub>		N <sub>1</sub>	N <sub>0</sub>	
S <sub>EE</sub> = 0	0	a = 00	S <sub>OE</sub> = 1	1	p = 0
S <sub>EE</sub> = 0	0	b = 01	S <sub>EO</sub> = 0	1	p = 0
S <sub>EE</sub> = 0	0	c = 10	S <sub>EE</sub> = 0	0	p = 0
S <sub>EO</sub> = 0	1	a = 00	S <sub>OO</sub> = 1	0	q = 1
S <sub>EO</sub> = 0	1	b = 01	S <sub>EE</sub> = 0	0	q = 1
S <sub>EO</sub> = 0	1	c = 10	S <sub>EO</sub> = 0	1	q = 1
S <sub>OO</sub> = 1	0	a = 00	S <sub>EO</sub> = 0	1	p = 0
S <sub>OO</sub> = 1	0	b = 01	S <sub>OE</sub> = 1	1	p = 0
S <sub>OO</sub> = 1	0	c = 10	S <sub>OO</sub> = 1	0	p = 0
S <sub>OE</sub> = 1	1	a = 00	S <sub>EE</sub> = 0	0	p = 0
S <sub>OE</sub> = 1	1	b = 01	S <sub>OO</sub> = 1	0	p = 0
S <sub>OE</sub> = 1	1	c = 10	S <sub>OE</sub> = 1	1	p = 0

# FSM EXAMPLES

## EXAMPLE #1

- The Boolean function for the output can be determined from a Karnaugh map as follows.
- Note that an input of **11** is not possible since we only have three inputs that we have assigned to **00**, **01**, and **10**. We can therefore use don't cares for this possible input.

$X_1X_0 \backslash P_1P_0$	00	01	11	10
00	0	1	0	0
01	0	1	0	0
11	X	X	X	X
10	0	1	0	0

$$Z = \overline{P_1}P_0$$

# FSM EXAMPLES

## EXAMPLE #1

- The Boolean function for the next state bit can also be determined from Karnaugh maps as follows.

		$P_1P_0$			
		00	01	11	10
$X_1X_0$	00	1	1	0	0
	01	0	0	1	1
	11	X	X	X	X
	10	0	0	1	1

$$N_1 = \overline{P_1 \oplus X_1 \oplus X_0}$$

		$P_1P_0$			
		00	01	11	10
$X_1X_0$	00	1	0	0	1
	01	1	0	0	1
	11	X	X	X	X
	10	0	1	1	0

$$N_0 = P_0X_1 + \overline{P_0}\overline{X_1} = \overline{P_0 \oplus X_1}$$

# FSM EXAMPLES


## EXAMPLE #1

- The following logic circuit can be made with these Boolean functions.

$$N_1 = \overline{P_1 \oplus X_1 \oplus X_0}$$

$$N_0 = \overline{P_0 \oplus X_1}$$

$$Z = \overline{P_1} P_0$$

 

- A sequential circuit is defined by the following Boolean functions with input  $X$ , present states  $P_0$ ,  $P_1$ , and  $P_2$ , and next states  $N_0$ ,  $N_1$ , and  $N_2$ .
  - $N_2 = X(P_1 \oplus P_0) + \overline{X(P_1 \oplus P_0)}$
  - $N_1 = P_2$
  - $N_0 = P_1$
  - $Z = XP_1P_2$
- Derive the state table.
- Derive the state diagram.

# FSM EXAMPLES

## EXAMPLE #2

- The state table is formed as follows.

Present State			Input X	Next State			Output Z
P <sub>2</sub>	P <sub>1</sub>	P <sub>0</sub>		N <sub>2</sub>	N <sub>1</sub>	N <sub>0</sub>	
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	0	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	0	1	0
0	1	1	1	0	0	1	0
1	0	0	0	1	1	0	0
1	0	0	1	0	1	0	0
1	0	1	0	0	1	0	0
1	0	1	1	1	1	0	0
1	1	0	0	0	1	1	0
1	1	0	1	1	1	1	1
1	1	1	0	1	1	1	0
1	1	1	1	0	1	1	1



# FSM EXAMPLES

## EXAMPLE #2

- The state diagram can be drawn as follows.

